

RGB Video Switching (Replacing the HC4053 and Buffer/Amplifier)

Switching Between Video Sources

It is becoming common practice to switch more than one video source. Pericom's *PI5V330 Quad 2-Channel Multiplexer/Demultiplexer* can replace both the HC4053 analog multiplexer and any buffer/amplifier chip (see Figures 1 and 3).

When using analog switches or multiplexers, with relatively high ON-resistance, it is often common to see a relatively high-insertion loss or voltage drop across the switch. For video applications, this on-resistance (R_{ON}) must be compensated by using a gain-stage buffer/amplifier. Since the PI5V330 has approximately $3\Omega R_{ON}$, industry standard current output RAMDACs can easily drive the switch and cable with minimal loss without the need for the buffer/amplifier.

Replacing HC4053

The HC4053 has typically $40\Omega R_{ON}$, while the PI5V330 has 3Ω . This reduction in R_{ON} results in a distortion decrease down to -28dB or four percent when the line termination is 75Ω . $\text{Distortion} = 20\text{LOG}(R_{ON}/R_L)$.

Replacing the Buffer/Amplifier

As mentioned previously, if the RAMDAC output compliance is not exceeded, it can supply enough current to drive the cable so the buffer/amplifier is no longer needed.

To ensure one LSB nonlinearity, this compliance is generally $+1.4\text{V}$. Figure 3 shows the voltage at the video input to be 1.08V , well within maximum compliance. Normally, the RAMDAC can drive 26.66mA into a doubly terminated resistor ($75\Omega/75\Omega = 37.5\Omega$). This conforms to the RS-343 specification. The PI5V330 has a drive-through current of 100mA .

1. Performs a current-to-voltage conversion.
 2. Matches the 75Ω cable impedance to reduce reflections.
- This video coax cable is generally only six-feet long.

PI5V330 Advantages in Video Application

- Ultra-low R_{ON}
- Crosstalk = 60dB @ 10MHz
- Single supply operation: $+5\text{V}$
- Wide bandwidth = 190MHz

Note that the PI5V330 can be used in SGA or SVGA (800×600), XGA (1024×768), or Hi Res (1500×1200 and beyond) resolutions where pixels need to be energized quickly.

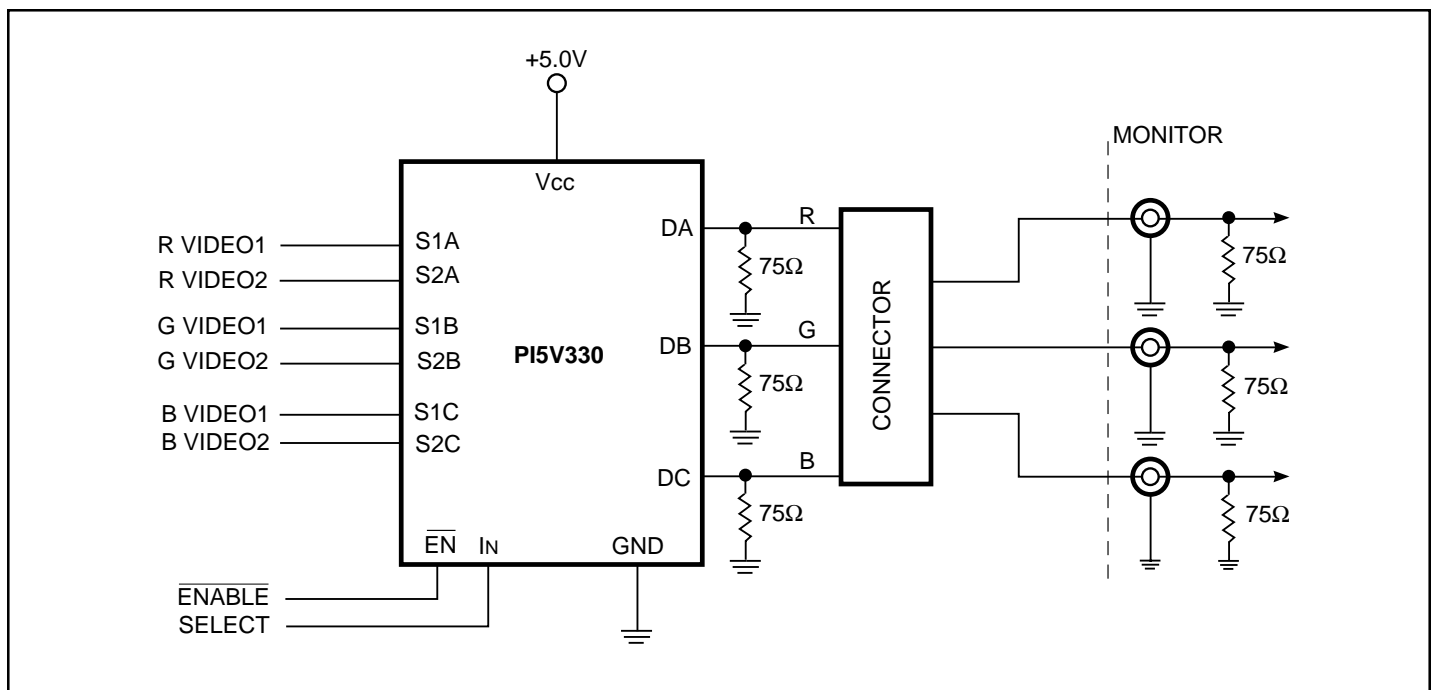


Figure 1. RGB Video Circuit (new design)

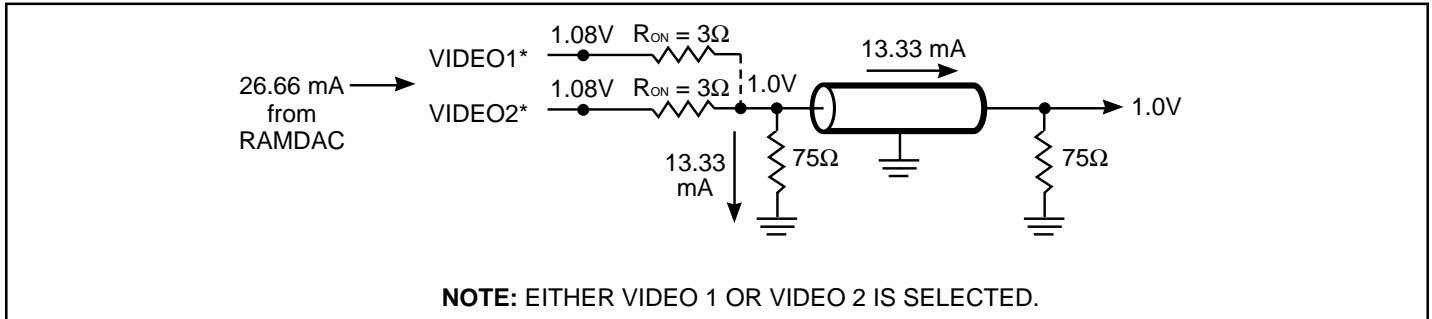


Figure 2. PI5V330 Drive-thru Current and Distortion Equivalent Circuit

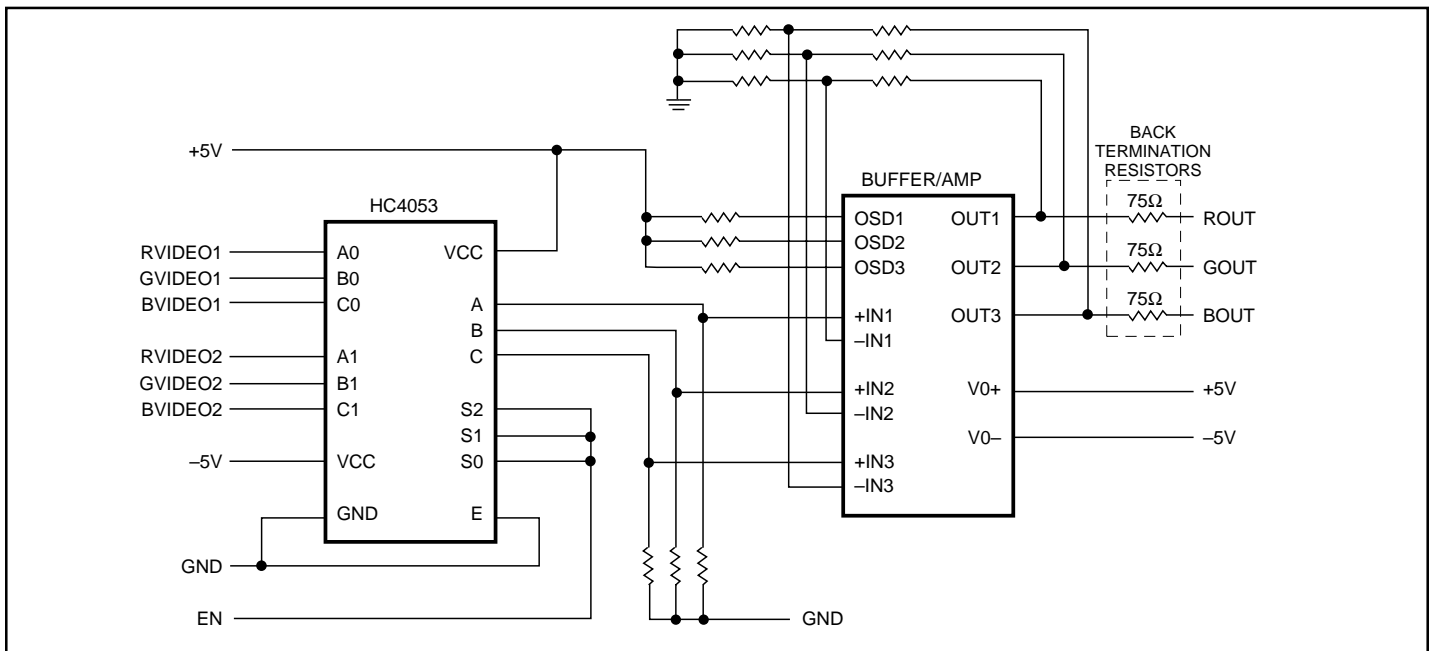


Figure 3. PI5V330 Replacement Circuit (old design)

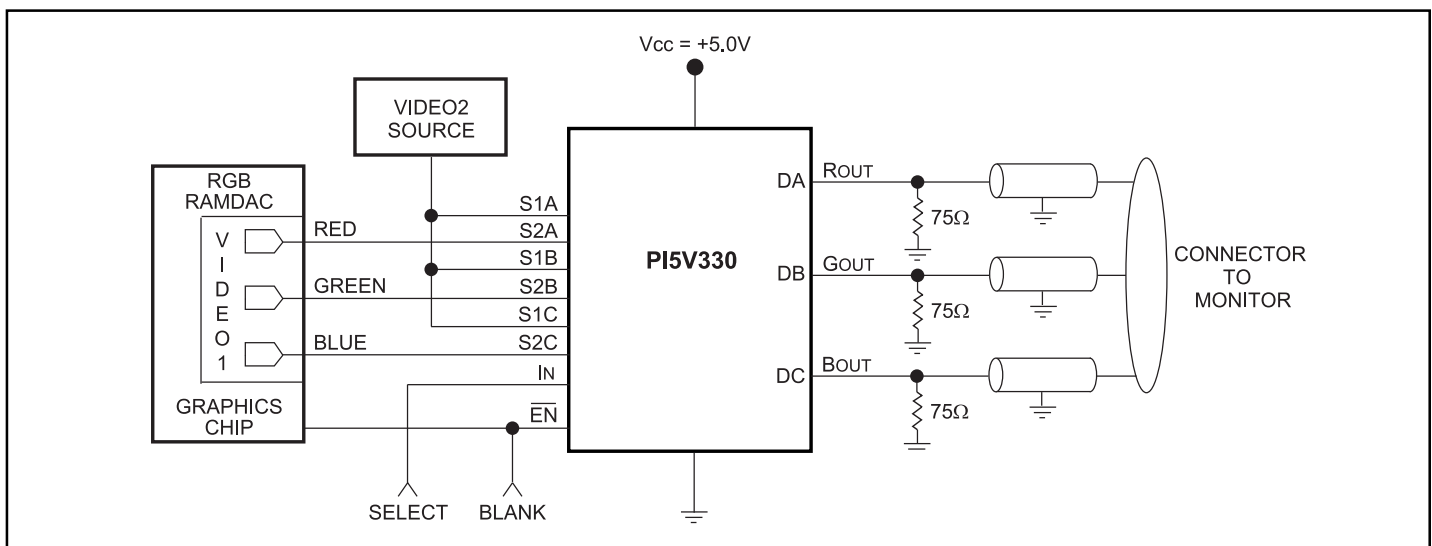


Figure 4. New System Circuit