

AN57

Automotive EMC considerations for switching regulator LED lighting applications using ZXLD1362

Adrian Wong, Systems Engineer, Diodes Incorporated


Introduction

This application note describes a driver solution developed using the Zetex ZXLD1362 LED driver IC for an automotive EMC compliant solution. ZXLD1362 switching regulator allows to maximize the efficiency gains offered by LED lighting solutions in automotive applications, while reducing the component count and the complexity of the circuit.

ZXLD1362 Description

The **ZXLD1362** hysteretic converter features can be summarized as:

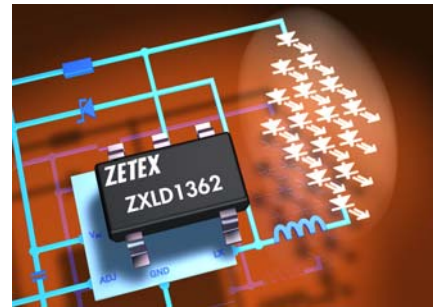- Wide input voltage range
- 7V to 60V; internal 60V NDMOS switch
- Up to 1A output current
- Capable of driving up to 16 series connected 3 Watt LEDs
- High efficiency (see datasheet - but >90% with 15 LEDs)
- Low quiescent current: (100uA typical)
- Brightness control using DC voltage or PWM (low or high frequency)
- Optional soft-start; up to 1MHz switching frequency



For more details about the hysteretic converter, please refer to the Zetex web site applications page.

Automotive EMC problems

Until now, wiring harnesses have been used to distribute power and signals throughout automotive systems. However, as can be seen in Figure 1, they are usually routed to accommodate long paths and remote LED lighting switching regulator locations are far away from the car battery. Moreover, they have parasitic inductances or capacitances which incur the adverse resonant effects associated with noise currents. As a result, there are two typical EMC problems arising with respective solutions as described in Table 1.

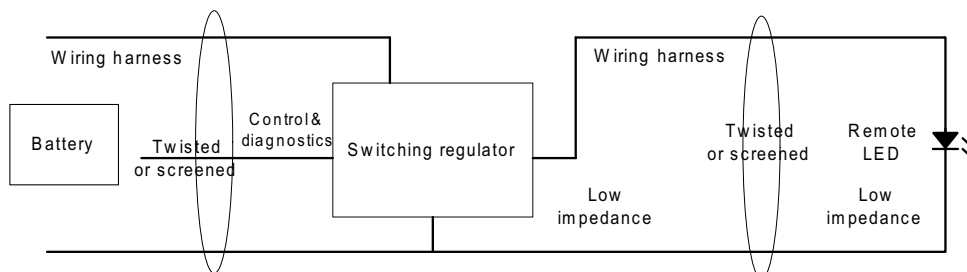


Figure 1 – A simple diagram showing remote LED from switcher

AN57

| Major problem | Solution(s) |
|----------------------------------|--|
| Conducted Emissions and Immunity | <ol style="list-style-type: none">1. A line filter is installed on the harness close to the emission source and away from the sensitive circuits by inserting a high impedance path to the noise current flow.2. It also minimizes the "cross talk" capacitive coupling from the device to the power supply wiring. |
| Radiated Emissions and Immunity | <ol style="list-style-type: none">1. Cables are shielded with the termination of a low impedance path for noise currents.2. Cables are twisted to minimize the loop area for the inductive noise coupling. |

Table 1 - Automotive EMC considerations

Instead of implementing all of the above common but costly measures, it is recommended to focus on suppressing the noise source as much as possible. In the application circuit shown in Figure 2, the necessary damping circuits are therefore incorporated around the LED lighting switching regulator. Also, the use of the fast hysteretic converter can dither the switching frequency, and benefit from a lower frequency operation, which attenuates the overall emissions.

Automotive EMC standards

EMC standards in automotive lighting applications are vehicle manufacturer dependent. Table 2 summarises the automotive test standards for a generic tier 1 car manufacturer. The tests cover the supply of electrical products to a vehicle manufacturer only and do not extend to whole vehicle testing, which remains exclusively the domain of the vehicle manufacturer.

| Automotive standard | Test(s) covered |
|---------------------|----------------------------------|
| CISPR-25 | Conducted and Radiated Emissions |
| ISO 11452-2 & -4 | Radiated Immunity |
| ISO 7637-2 | Conducted Transient Immunity |
| ISO 10605 | Electrostatic Discharge |

Table 2 - Automotive test standards

The impact of operating frequency and switching topology

The choice of operating frequency and type of switching topology is important from an EMC perspective since they can yield quite different EMI performance. It is often desirable from space and cost considerations to choose a high frequency switching regulator with small inductors. However the fast edges associated with high frequency switches can cause harmonics that are difficult to damp down - a prerequisite if conducted and radiated tests are not to be failed.

Simpler hysteretic converters offer a variable frequency output, which if handled with care can produce an inherent spread spectrum response that reduces average radiated and conducted emissions. If noise filters are needed then the lowest operating frequency needs to be known to design a suitable filter.

ESD and RF immunity considerations

Switching regulators are no different from any other analogue circuit with respect to ESD. Normal system considerations should be taken into account to ensure the circuit is shielded or protected by suitable ESD diodes. The same is true for RF, although the RF levels in automotive tests are much more severe than in commercial and industrial environments. Low impedances are more immune than high impedances. This is particularly important on dimming control and status pins.

Interior lighting application using ZXLD1362

Figures 2 and 3 show the schematic and the board view of a 350mA LED driver circuit using ZXLD1362, for car interior lighting respectively. The circuit is intended to be implemented with the LED remote from the switching circuit which is also connected to the battery via long wires.

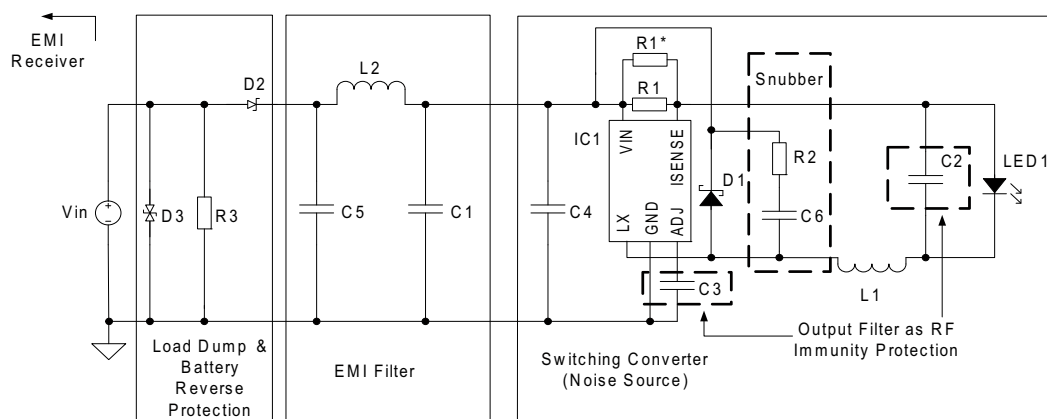


Figure 2 - Circuit diagram of a ZXLD1362 LED driver for car interior lighting

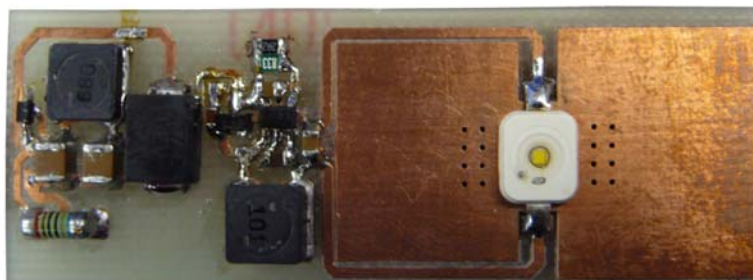


Figure 3 - Circuit board view

AN57

EMC measures for ZXLD1362 hysteretic converter

In order to properly dissipate the heat generated by a power LED, it is often required to expose an adequate copper area on both sides of the PCB together with a number of interconnecting thermal vias for soldering and heat transfer. As a result, the routing of a long path to the LED is unavoidable. So a capacitor C_2 is added not only to reduce the LED ripple current but also to filter its noise current. In some worst cases, an extra common mode choke may need to be inserted.

For this lighting solution a 60V ZXLD1362 based buck converter employing hysteretic current control was used. With reference to Figure 2 the full EMC solution consists of the following measures: For load dump protection a bidirectional transient suppressor diode D_3 is added. Its fast instantaneous clamping response to high transient over-voltages with high peak pulse power makes it ideally suited to this particular function. The EMI filter consists of an inductor L_2 and two capacitors C_1 and C_5 that form a simple II filter which attenuates the conducted EMI. A capacitor C_3 of 10nF is connected from ADJ pin to ground to filter noise pickup which may create flickering during the immunity test. An optional basic RC snubber (R_2 - C_6) could be connected across the diode D_1 to control both the spike's transition rate and shape. The capacitor controls the rise time and the resistor the peak voltage. In fact this was not required to meet the EMC test conditions but EMC measures are better to be designed in and removed rather than retrofitted. Cores of both the switching inductor L_1 and the filter inductor L_2 are shielded, ferrite-based and closed magnetic field type, in order to provide suppression of radiated emissions as well as immunity to external fields.

EMI filter design analysis

ZXLD1362 is a hysteretic LED driver that guarantees a constant current on the LED with a very simple circuit. The hysteretic converter is a variable frequency topology. EMI filters need to be designed to take into account the lowest operating frequency. In order to successfully attenuate the switcher noise a 4th-order low-pass II filter, is formed by C_5 , L_2 and C_1 . The filter offers more than 60dB attenuation at 300 kHz according to the transfer function analysis using Millman's Theorem. The resulting filter attenuation is also shown in Figure 4.

$$\frac{V_O(s)}{V_I(s)} = \frac{1}{L_S L_2 C_1 C_5} \left[\frac{1}{s^4 + \frac{1}{C_5 R_L} s^3 + \left(\frac{1}{L_S C_1} + \frac{1}{L_2 C_1} + \frac{1}{L_2 C_5} \right) s^2 + \frac{1}{C_1 C_5 R_L} \left(\frac{1}{L_S} + \frac{1}{L_2} \right) s + \frac{1}{L_S L_2 C_1 C_5}} \right]$$
$$= 1.331 \times 10^{23} \left(\frac{1}{s^4 + 4.256 \times 10^{13} s^2 + 1.331 \times 10^{23}} \right) \quad \text{For } R_L \gg 1$$

where:

$V_I(s)$ stands for the noise source

$V_O(s)$ stands for the EMI receiver

R_L accounts for the loading impedance of the EMI receiver

L_S accounts for the parasitic trace inductance

In this example, we have

$$L_2=68\mu\text{H}; C_1=C_5=4.7\mu\text{F}; L_S=5\text{nH}$$

In the circuit, the switching frequency at $V_{IN}=12\text{V}$ is calculated to be about 300 kHz based on the below derivation with reference to the ZXLD1362 internal block diagram as shown in the datasheet.

$$f_{\text{SW}} = \frac{1}{\frac{L\Delta I}{V_{IN} - V_{\text{LED}} - I_{\text{AVG}}(R_S + rL + R_{\text{LX}})} + \frac{L\Delta I}{V_{\text{LED}} + V_D + I_{\text{AVG}}(R_S + rL)} + 2T_{\text{PD}}}$$

where:

L is the coil inductance (H)

rL is the coil resistance (Ω)

I_{AVG} is the required LED current (A)

ΔI is the coil peak-peak ripple current (A) {Internally set to $0.3 \times I_{\text{AVG}}$ }

V_{IN} is the supply voltage (V)

V_{LED} is the total LED forward voltage (V)

R_{LX} is the switch resistance (Ω)

V_D is the diode forward voltage at the required load current (V)

T_{PD} is the internal comparator propagation delay

The following necessary parameters are used for the substitution into the above equation.

$$L=L_1=100\mu\text{H}$$

$$rL=0.48\Omega$$

$$I_{\text{AVG}}=348.5\text{mA}$$

$$\Delta I=104.5\text{mA}$$

$$V_{IN}=12\text{V}$$

$$V_{\text{LED}}=3.8\text{V}$$

$$R_{\text{LX}}=1.5\Omega$$

$$V_D=375\text{mV at } I_F=348.5\text{mA}$$

$$R_S=R_1//R_1^*=0.33\Omega//2.2\Omega=0.287\Omega$$

$$T_{\text{PD}}=200\text{ns}$$

As such, the filter has been optimized to provide enough attenuation at the fundamental frequency as well as its harmonics in order to meet the conducted EMI requirement only with the simplest structure.

AN57

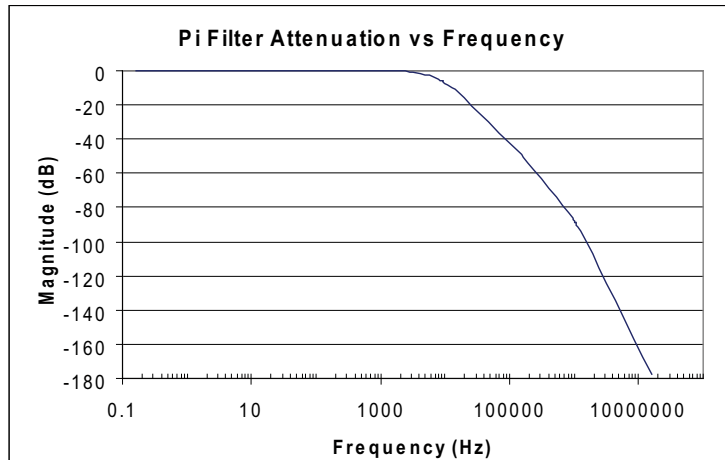


Figure 4 - Π filter attenuation vs frequency

Results/graphs for EMI and susceptibility

The EMC test results are shown in Figures 5, 6 and 7 in accordance with the following automotive standards with limit lines identified by the customer.

CISPR-25: Conducted and radiated emissions (Europe and Worldwide standards)

ISO11452: Radiated immunity (North America and Worldwide standards)

95/54/EC: Radiated emissions (European standards)

It should be noted that the radiated immunity test is correlated by the strip-line measurement inside a GTEM cell while the radiated emission test is correlated by the absorber chamber verification using an active loop antenna at 1m range.

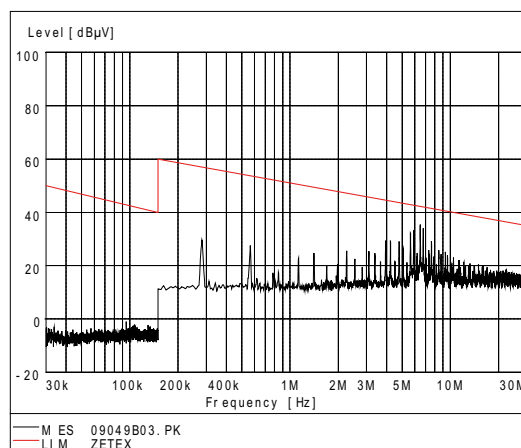


Figure 5 - Conducted EMI scan

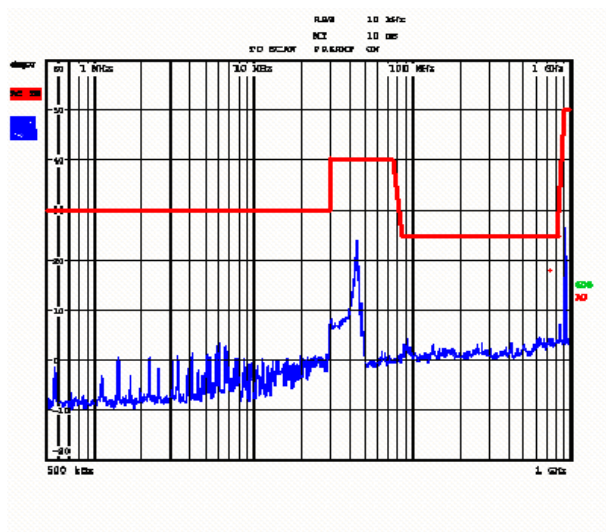


Figure 6 – Operating emission using GTEM


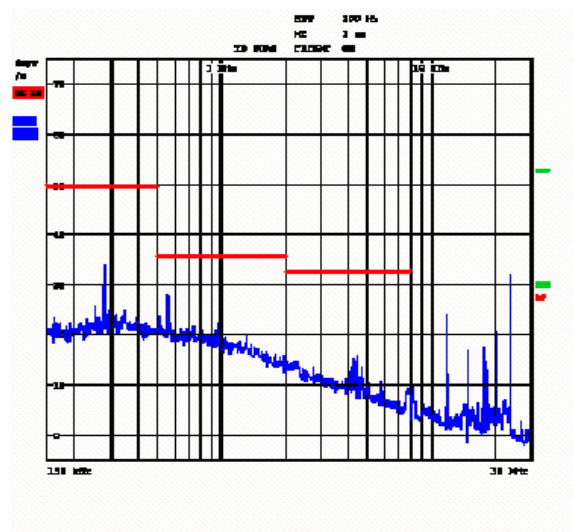



Figure 7- Operating emission with loop antenna in 1m range

PCB layout considerations and bill of materials

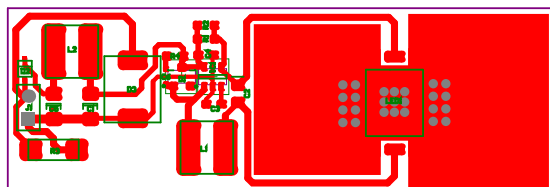In designing for EMC, PCB layout plays a critical role in producing an effective solution. For this design the following measures were taken as implemented in Figure 8.



Top copper silkscreen

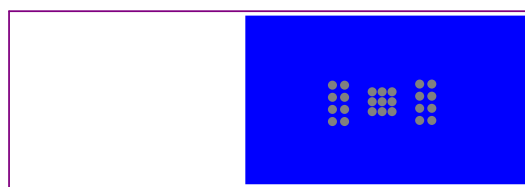

Bottom copper silkscreen

Figure 8 - Circuit layout

AN57

- The capacitor C_3 connected from ADJ pin to ground is as short as possible.
- The high di/dt loop ($L_X-D_1-V_{IN}-C_4$) with a fast switching current is made as small as possible. This minimises the differential mode noise related the loop inductance multiplied by the fast transient switching ($L \cdot di/dt$).
- A simple Π filter ($C_5-L_2-C_1$) is placed as close as possible to the input terminals performing the optimal conducted EMI attenuation.
- The perpendicular configuration of the EMI filter components lowers the capacitive coupling between the inductor and capacitors.
- A V-connection of the filter capacitors C_1 and C_5 helps prevent self resonance and so avoids degrading the EMI performance.
- Careful component placement avoids the mutual coupling of noise generating nodes to noise sensitive nodes.

| Ref. | Value | Package | Part number | Manufacturer | Description |
|-----------|-----------------|----------|--------------------|------------------|--|
| C1, C5 | 4.7 μ F/50V | 1210 | GRM32ER71H475KA88 | Murata | SMD capacitor |
| C2 | 1 μ F/25V | 0805 | GRM21BR71E105K | Murata | SMD capacitor |
| C3 | 10nF/50V | 0805 | GRM21BR71H103K | Murata | SMD capacitor |
| C4 | 0.1 μ F/50V | 0603 | GCM188R71H104KA57 | Murata | SMD capacitor |
| C6 | Open | 0603 | B37931-K5XXX-K70 | Murata | SMD capacitor |
| D1 | 40V/1.16A | SOT23 | ZLLS1000 | Diodes Inc | Low leakage schottky diode |
| D2 | 40V/0.52A | SOD323 | ZLLS400 | Diodes Inc | Low leakage schottky diode |
| D3 | N/A | SMC | SMCJ36CA | Diodes Inc | SMD bidirectional transient voltage suppressor |
| IC1 | N/A | TSOT23-5 | ZXLD1362 | Diodes Inc | 1A LED driver with internal switch |
| L1 | 100 μ H | Type LH | WE-TPC 744053101 | Würth Elektronik | SMD-shielded tiny power inductor |
| L2 | 68 μ H | Type L | WE-TPC 744052680 | Würth Elektronik | SMD-shielded tiny power inductor |
| LED 1 | N/A | SMD CLC | LW W5SM | Osram | Golden Dragon |
| R1 | 0.33 Ω | 0805 | RL1220S-R33 | Cyntec | SMD resistor |
| R1* | 2.2 Ω | 0805 | RL1220-2R2 | Cyntec | SMD resistor |
| R2 | Open | 0805 | RL1220S-XXX | Cyntec | SMD resistor |
| R3 | 680 Ω | MELF | SMM0207 50 680R 1% | Vishay | Metal film, cylindrical resistor |

Table 3 - Bill of materials

Conclusion

Successful implementation of a switching regulator to drive LEDs can be achieved in the tough automotive environment using ZXLD1362. Defensive measures must be designed to cope with conductive and radiated emissions as well as creating a robust RF immune system.

Since the choice of topology, circuit design and PCB layout are essential to ensure the lighting solution operates correctly in an automotive application, this application note described how to manage these tasks using the ZETEX LED driver ZXLD1362.

AN57

Definitions

Product change

Diodes Incorporated reserves the right to alter, without notice, specifications, design, price or conditions of supply of any product or service. Customers are solely responsible for obtaining the latest relevant information before placing orders.

Applications disclaimer

The circuits in this design/application note are offered as design ideas. It is the responsibility of the user to ensure that the circuit is fit for the user's application and meets with the user's requirements. No representation or warranty is given and no liability whatsoever is assumed by Diodes Inc. with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Diodes Inc. does not assume any legal responsibility or will not be held legally liable (whether in contract, tort (including negligence), breach of statutory duty, restriction or otherwise) for any damages, loss of profit, business, contract, opportunity or consequential loss in the use of these circuit applications, under any circumstances.

Life support

Diodes Zetex products are specifically not authorized for use as critical components in life support devices or systems without the express written approval of the Chief Executive Officer of Diodes Incorporated. As used herein:

A. Life support devices or systems are devices or systems which:

1. are intended to implant into the body

or

2. support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labelling can be reasonably expected to result in significant injury to the user.

B. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or to affect its safety or effectiveness.

Reproduction

The product specifications contained in this publication are issued to provide outline information only which (unless agreed by the company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned.

Terms and Conditions

All products are sold subjects to Diodes Inc. terms and conditions of sale, and this disclaimer (save in the event of a conflict between the two when the terms of the contract shall prevail) according to region, supplied at the time of order acknowledgement.

For the latest information on technology, delivery terms and conditions and prices, please contact your nearest Diodes Zetex sales office .

Quality of product

Diodes Zetex Semiconductors Limited is an ISO 9001 and TS16949 certified semiconductor manufacturer.

To ensure quality of service and products we strongly advise the purchase of parts directly from Diodes Incorporated or one of our regionally authorized distributors. For a complete listing of authorized distributors please visit: www.diodes.com or www.zetex.com
Diodes Incorporated does not warrant or accept any liability whatsoever in respect of any parts purchased through unauthorized sales channels.

ESD (Electrostatic discharge)

Semiconductor devices are susceptible to damage by ESD. Suitable precautions should be taken when handling and transporting devices. The possible damage to devices depends on the circumstances of the handling and transporting, and the nature of the device. The extent of damage can vary from immediate functional or parametric malfunction to degradation of function or performance in use over time. Devices suspected of being affected should be replaced.

Green compliance

Diodes Zetex Semiconductors is committed to environmental excellence in all aspects of its operations which includes meeting or exceeding regulatory requirements with respect to the use of hazardous substances. Numerous successful programs have been implemented to reduce the use of hazardous substances and/or emissions.

All Diodes Zetex components are compliant with the RoHS directive, and through this it is supporting its customers in their compliance with WEEE and ELV directives.

Product status key:

| | |
|-----------------------------------|--|
| "Preview" | Future device intended for production at some point. Samples may be available |
| "Active" | Product status recommended for new designs |
| "Last time buy (LTB)" | Device will be discontinued and last time buy period and delivery is in effect |
| "Not recommended for new designs" | Device is still in production to support existing designs and production |
| "Obsolete" | Production has been discontinued |

Datasheet status key:

| | |
|-----------------------|---|
| "Draft version" | This term denotes a very early datasheet version and contains highly provisional information, which may change in any manner without notice. |
| "Provisional version" | This term denotes a pre-release datasheet. It provides a clear indication of anticipated performance. However, changes to the test conditions and specifications may occur, at any time and without notice. |
| "Issue" | This term denotes an issued datasheet containing finalized specifications. However, changes to specifications may occur, at any time and without notice. |

Diodes Zetex sales offices

| Europe | Americas | Asia Pacific | Corporate Headquarters |
|--|---|---|---|
| Zetex GmbH Kustermann-park Balanstraße 59 D-81541 München Germany Telephone: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 europe.sales@zetex.com | Zetex Inc 700 Veterans Memorial Highway Hauppauge, NY 11788 USA Telephone: (1) 631 360 2222 Fax: (1) 631 360 8222 usa.sales@zetex.com | Diodes Zetex (Asia) Ltd 3701-04 Metroplaza Tower 1 Hing Fong Road, Kwai Fong Hong Kong Telephone: (852) 26100 611 Fax: (852) 24250 494 asia.sales@zetex.com | Diodes Incorporated 15660 N Dallas Parkway Suite 850, Dallas TX75248, USA Telephone: (1) 972 385 2810 www.diodes.com |

© 2007 Published by Diodes Incorporated 2008