



C76-C83 are "must have" to prevent non-DP compliant 3.3V signals from plug-in as real-seen-case.

No-chokes between 30532 and type-C connector, because 30532 is a passive switch without EMI issue.

Use 0.22uf if output swing >1.2V or using re-drivers

See source truth table for the control of CONF[2:0]

**PI3USB30532 reference schematic for source application**

Contact Diodes local sales for TVS